

# 计算机组织与结构 II：POC 实验报告

李勃璘

东南大学

日期：2025 年 3 月 18 日

## 摘 要

本文为计算机组织与结构 II 课程设计中，8 位并行输出控制单元（Parallel Output Controller, POC）的说明文档。该控制单元的状态和输入数据受一 8 位处理器控制，并可以与打印机交互，将内部数据打印出来。项目源代码已附在文末。

## 1 整体功能

本设计实现了一个 8-bit 的并行输出控制单元，其通过一个简易的 8-bit 处理器获取数据和控制信息，并将输出结果传输给打印机模块。打印机经过一段时间的延时后将数据打印出来。项目的总体结构如图 1 所示。

 


图 1: 项目模块结构

## 2 POC 模块

该模块完成并行输出控制单元（下文称 POC）的描述，以及和打印机（下文称 PRINTER）、处理器（下文称 PROCESSOR）的交互。

### 2.1 时钟与复位信号

该模块的时钟和复位信号如表 1。

信号名	位宽	流向	描述
i_clk	1	输入	时钟信号
i_rst_n	1	输入	全局异步复位

表 1: POC 模块的时钟与复位信号

## 2.2 模块接口

该模块的对外接口如表 2。

端口	位宽	流向	描述	来源/通向模块
i_addr	1	输入	地址信号，当值为 0 时，i_din 被解释为状态信号； 当值为 1 时，被解释为要打印的数据	PROCESSOR
o_dout	8	输出	输出自身状态信号	PROCESSOR
i_din	8	输入	数据信号，值意义参考 i_addr 的值	PROCESSOR
i_rw	1	输入	读写信号，当值为 1 时 PROCESSOR 向 POC 写值	PROCESSOR
i_mode	1	输入	模式选择，1 为中断模式，0 为查询模式	/
o_irq	1	输出	中断信号，为 1 时向 PROCESSOR 发出中断请求（低有效）	PROCESSOR
i_rdy	1	输入	信号为 1 时允许向打印机写数据	PRINTER
o_tr	1	输出	信号为 1 时向打印机发送请求	PRINTER
o_pd	8	输出	向打印机输出数据	PRINTER

表 2: POC 模块端口说明

## 2.3 模块功能描述

该模块描述了查询模式和中断模式下的 POC 状态转换和信号输入输出。模块功能见算法 1。<sup>1</sup>实际实现时，为调试方便以及区分两种模式下的功能，为中断模式下的数据更新和打印机交互各设立了一个状态，但功能完全相同。

<sup>1</sup>表述和代码不完全相同。

---

**Algorithm 1** POC 模块

---

```
1: Note: System turns query mode when  $SR_0$  is 0, otherwise it turns to interrupt mode.
2: Input:  $i\_clk, i\_rst\_n, i\_mode, i\_rw, i\_addr, i\_din, i\_rdy$ 
3: Output:  $o\_dout, o\_irq, o\_tr, o\_pd$ 
4: Internal Registers:  $state, buffer, status, printer\_data, enable\_printer, ready$ 
5: procedure INITIALIZE
6:    $state \leftarrow$  Wait for PROCESSOR data
7:    $ready \leftarrow 0$ 
8:    $status \leftarrow 8'b10000000$ 
9:    $enable\_printer \leftarrow 0$ 
10:   $interrupt \leftarrow SR_7 \& SR_0$ 
11:   $SR_0 \leftarrow i\_mode$ 
12: end procedure
13: procedure WAIT FOR PROCESSOR DATA
14:   State Transition:
15:   if  $i\_rw == 1 \&\& SR_0 == 0$  or  $interrupt$  then
16:      $state \leftarrow$  Update buffer and status from PROCESSOR
17:   end if
18: end procedure
19: procedure UPDATE BUFFER AND STATUS FROM PROCESSOR
20:   if  $i\_rw == 1$  then
21:     if  $i\_addr == 1$  then
22:        $buffer \leftarrow i\_din$ 
23:     else if  $i\_addr == 0$  then
24:        $status \leftarrow i\_din$ 
25:     end if
26:   end if
27:   State Transition:
28:   if  $SR_7 == 0$  then
29:      $state \leftarrow$  Push buffer to PRINTER
30:   end if
31: end procedure
32: procedure PUSH BUFFER TO PRINTER
33:   if PRINTER Ready then
34:      $printer\_data \leftarrow buffer$  (Until the end of the state)
35:      $o\_tr \leftarrow$  pulse
36:     State Transition:
37:      $state \leftarrow$  Wait for PROCESSOR data
38:   end if
39: end procedure
```

---

## 3 PROCESSOR 模块

### 3.1 时钟与复位信号

该模块的时钟和复位信号如表 3。

信号名	位宽	流向	描述
i_clk	1	输入	时钟信号
i_rst_n	1	输入	全局异步复位

表 3: POC 模块的时钟与复位信号

### 3.2 模块接口

该模块的对外接口如表 4。

端口	位宽	流向	描述	来源/通向模块
o_addr	1	输出	地址信号，当值为 0 时，i_din 被解释为状态信号； 当值为 1 时，被解释为要打印的数据	POC
i_dout	8	输入	POC 的 8 位状态信号 (SR)	POC
o_din	8	输出	数据信号，值意义参考 o_addr 的值	POC
o_rw	1	输出	读写信号，当值为 1 时 PROCESSOR 向 POC 写值	POC
i_irq	1	输入	来自 POC 的中断信号 (低有效)	POC
i_data	8	输入	系统输入数据 (将被打印)	/

表 4: PROCESSOR 模块端口说明

### 3.3 模块功能描述

该模块描述了一个中央处理器（模块功能如算法 2）。它向 POC 传递数据，并在传递数据结束后将  $SR_7$  归零以表征传送结束。处理器使用地址线选择要写入的寄存器，使用数据线写入数据。地址译码与数据分配由 POC 完成。

由于状态和数据共用一条传输线，有必要规定传送时序。规定当 POC 空闲时 ( $SR_7$  为 1)，先写入数据到传输线端口，然后打开写模式以更新传输线；更新之后等待一个周期，更改地址为“状态”，并写入更新  $SR_7$  后的状态数据。

---

**Algorithm 2** PROCESSOR 模块

---

```
1: Note: We denote STATUS as 0 and BUFFER as 1, as they represent the actual bit allocation.
2: Input:  $i\_clk, i\_rst\_n, i\_irq, i\_dout, i\_data$ 
3: Output:  $o\_din, o\_addr, o\_rw$ 
4: Internal Registers:  $poc\_status, address, rw, state, next\_state, set\_data\_done, read\_status\_done$ 
5: procedure INITIALIZE( )
6:    $state \leftarrow IDLE$ 
7:    $poc\_status \leftarrow 8'b0$ 
8:    $read\_status\_done \leftarrow 0$ 
9: end procedure
10: procedure STATE TRANSITION( )
11:   if  $state == IDLE$  then
12:      $(Mode == Interrupt)?state \leftarrow READ\_FROM\_POC : state \leftarrow SET\_DATA$ 
13:   end if
14:    $state \leftarrow READ\_FROM\_POC \leftarrow SET\_DATA$ 
15:    $state \leftarrow WRITE\_DATA \leftarrow DELAY \leftarrow WRITE\_STATUS$ 
16:    $state \leftarrow IDLE$ 
17: end procedure
18: procedure CONTROL LOGIC FOR ADDRESS AND READ-WRITE( )
19:   state == IDLE:  $address \leftarrow STATUS, rw \leftarrow 0$ 
20:   state == READ\_FROM\_POC:  $rw \leftarrow 0, address \leftarrow STATUS$ 
21:   state == SET\_DATA:  $rw \leftarrow 0, address \leftarrow BUFFER$ 
22:   state == WRITE\_DATA:  $rw \leftarrow 1, address \leftarrow BUFFER$ 
23:   state == WRITE\_STATUS:  $rw \leftarrow 1, address \leftarrow STATUS$ 
24: end procedure
25: procedure DATA OUTPUT CONTROL( )
26:   if  $address == STATUS$  then
27:      $o\_din \leftarrow poc\_status$ 
28:   else
29:      $o\_din \leftarrow i\_data$ 
30:   end if
31: end procedure
32: procedure STATUS OPERATIONS( )
33:   if  $state == READ\_FROM\_POC$  then
34:      $poc\_status \leftarrow i\_dout$ 
35:   else if  $state == SET\_DATA$  then
36:      $poc\_status[7] \leftarrow 0$ 
37:   end if
38: end procedure
```

---

## 4 PRINTER 模块

### 4.1 时钟与复位信号

该模块的时钟和复位信号如表 1。

信号名	位宽	流向	描述
i_clk	1	输入	时钟信号
i_rst_n	1	输入	全局异步复位

表 5: PRINTER 模块的时钟与复位信号

### 4.2 模块接口

该模块的对外接口如表 6。

端口	位宽	流向	描述	来源/通向模块
i_tr	1	输入	冲激信号，象征打印开始	POC
i_pd	8	输入	POC 的 8 位待打印数据，打印机将取冲激信号为 1 时刻的输入	POC
o_rdy	1	输出	打印机工作时为 0，否则为 1	POC
o_data	8	输出	打印机输出打印数据	/

表 6: PRINTER 模块端口说明

### 4.3 模块功能描述

该模块是一个打印机模块。在接收到来自 POC 的冲激信号之后，打印机将自身状态设置为 BUSY。打印机需要 8 个时钟周期进行打印，打印的结果会延迟 4 个时钟。

---

**Algorithm 3** PRINTER 模块

---

```
1: Note: We denote STATUS as 0 and BUFFER as 1, as they represent the actual bit allocation.
2: Input:  $i\_clk, i\_rst\_n, i\_tr, i\_pd$ 
3: Output:  $o\_data, o\_rdy$ 
4: procedure IDLE()
5:   Do nothing.
6:    $o\_rdy \leftarrow 1$ 
7:   State Transition:
8:   if  $i\_tr == 1$  then
9:      $o\_rdy \leftarrow 0$  (with one clock cycle delay)
10:     $state \leftarrow BUSY$ 
11:  end if
12: end procedure
13: procedure BUSY()
14:  if  $counter == 8$  then
15:    End of printing.
16:     $state \leftarrow IDLE$ 
17:  else
18:    Print data with a delay of 4 clock cycles.
19:     $counter++$ ;
20:  end if
21: end procedure
```

---

## 5 仿真验证

### 5.1 时延分析

定义一个打印周期为从 POC 重置自身  $SR_7$  到一轮打印结束所经历的时钟上升沿个数。那么：

1. 由 POC 重置到 PROCESSOR 置零  $SR_7$ ，使用 6 个时钟，分别为读取 POC 信号的一个时钟和状态机的五个时钟；<sup>2</sup>
2. POC 此时开始与打印机进行交互。写入  $o\_tr$  和  $o\_pd$  共使用 1 个时钟， $o\_tr$  信号持续 1 个时钟；
3. 打印机收到信号后，耗时 8 个时钟打印数据；
4. 打印结束后，POC 重置  $SR_7$ ，使用 1 个时钟。

故一个打印周期为 17 个时钟（查询模式）或 16 个时钟（中断模式）。

### 5.2 激励设置


为了制造连续数据，避免数据丢包，输入数据的持续时间（延迟）应当和打印周期相同。仿真设置时钟以 20ns 为周期，故查询模式下，每一个数据更新之间的延迟应为 340ns；中孤单模式下，每一个数据更新之间的延迟应为 320ns。为简单起见，对两个不同的模式测试时，使用相同的测试样例。最终，选取无符号十进制数 0-20 按照 340ns/320ns 延时循环出现，作为仿真的输入数据。

<sup>2</sup>中断模式较查询模式少用一个时钟。因为中断信号由组合逻辑生成，中断模式下 PROCESSOR 可立刻读取中断信号，无需读取 POC 信号。

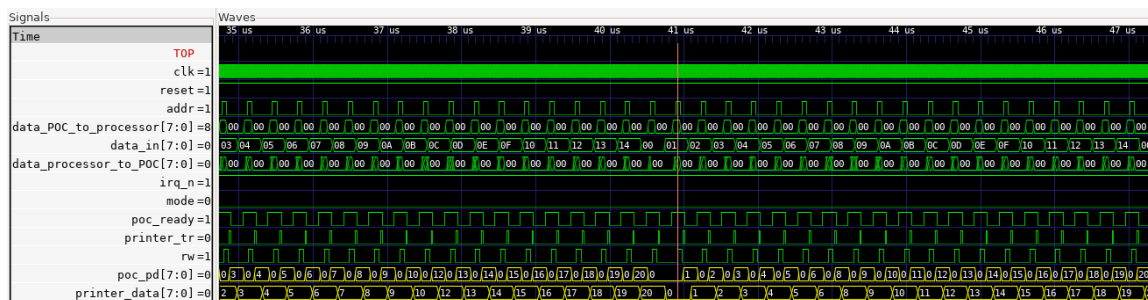
### 5.3 仿真结果

依据激励设置，撰写 POC 模块的 Testbench 如附录 A.5。使用 iverilog+vvp+gtkwave 运行仿真，运行结果为所有模块完整的波形图。

观察 TOP 模块的波形，可以看到查询和中断模式下（图 2），信号都能够流水输出，这证明激励设置正确。中断模式下中断信号在每个周期开始时由 POC 置零一次，标志一个打印周期的开始；而查询模式下中断信号始终为高电平，这符合我们的预期。



(a) 查询模式波形图

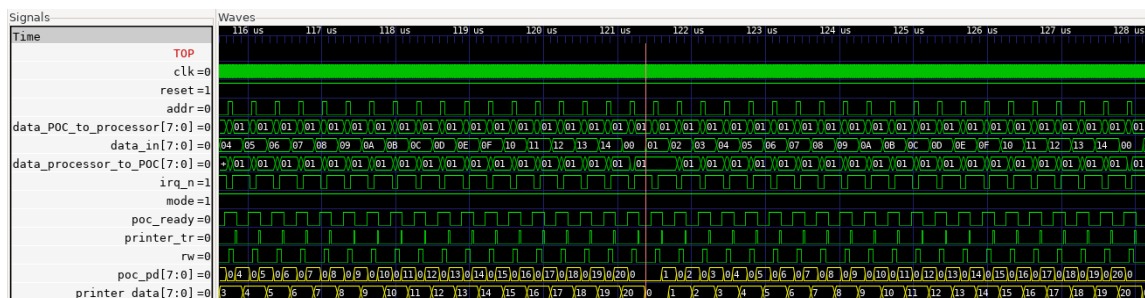

(b) 中断模式波形图

图 2: TOP 模块仿真波形图

接下来观察各个子模块的波形，验证时延分析的分析结果。*i\_dout* 是 POC 目前的状态，当 POC 将状态更新为 1 时，查询模式下 PROCESSOR 使用了 6 个时钟周期将 *SR<sub>7</sub>* 更新为 0。波形结果如图 3 所示。

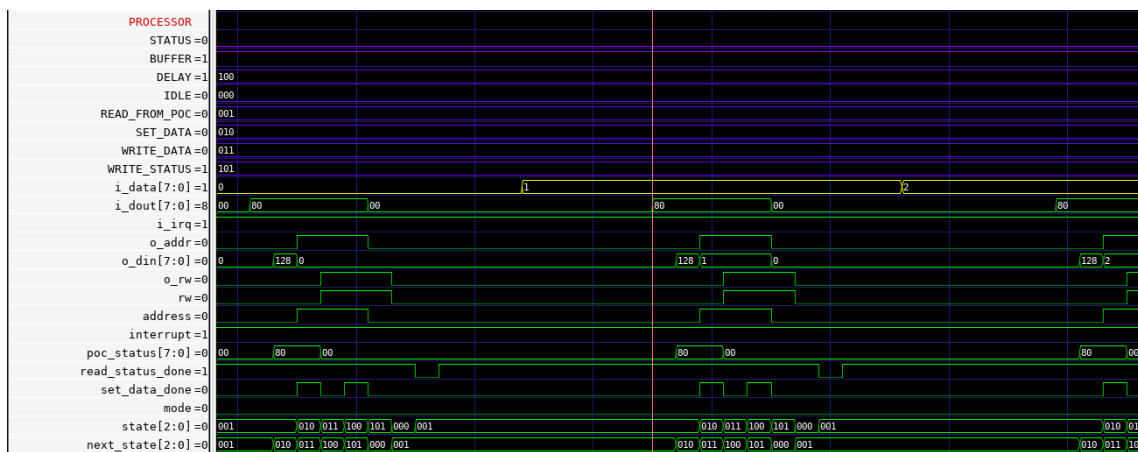


图 3: PROCESSOR 模块一个打印周期内的波形（查询模式）



中断模式下，PROCESSOR 使用了 5 个时钟周期将  $SR_7$  更新为 0（图 4）。

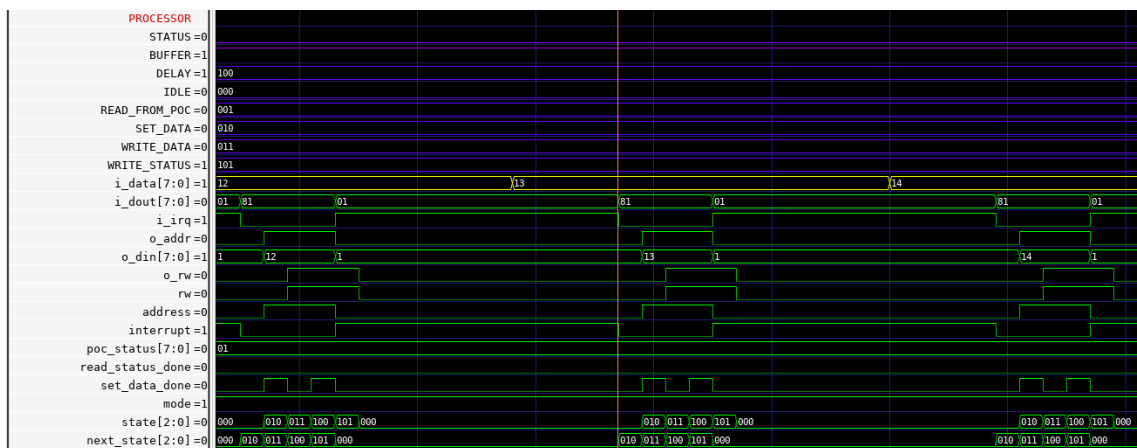


图 4: PROCESSOR 模块一个打印周期内的波形（中断模式）

POC 的  $SR_7$  被更新为 0 后，POC 使用一个时钟周期将  $o\_tr$  值赋为 1。 $o\_tr$  持续了一个时钟周期（图 5）。

 


图 5: POC 模块与 PRINTER 模块的交互

$o\_tr$  的脉冲使得打印机开始打印。打印机选取了  $o\_tr$  为 1 时的待打印数据，延迟四个周期后输出到  $o\_data$  中。打印机在开始打印时即开始计数。计数器  $counter$  满 8 之后归零，打印机的  $ready$  信号重新置 1。（图 6）

 


图 6: PRINTER 模块打印捕获的数据

POC 模块发现  $ready$  信号和寄存器中  $ready$  信号不同，即可判定打印结束。再经过一个周期后，POC 模块将自身  $SR_7$  置 1，打印周期结束。（图 7）

综上所述，总时钟周期和理论分析相同，这代表硬件实现的结果和预期相符。

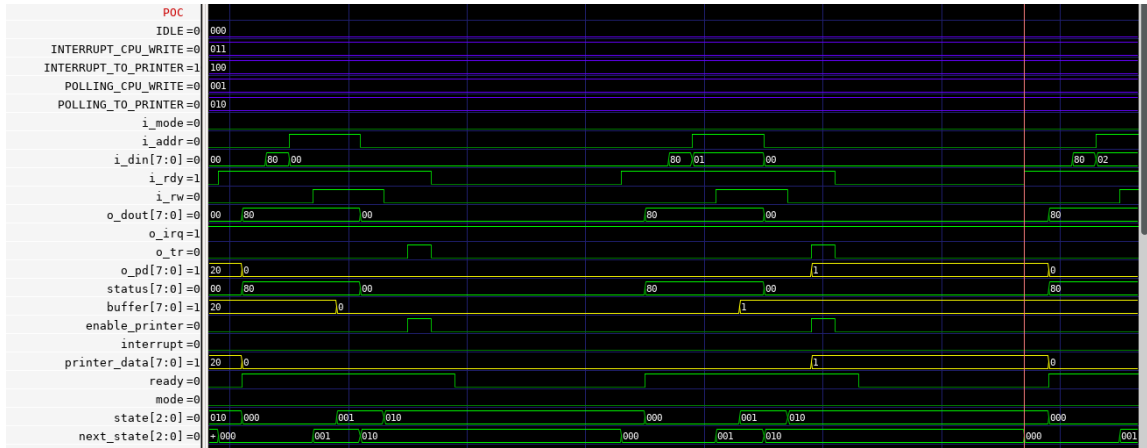


图 7: POC 模块更新  $SR_7$

## A 完整设计代码

完整代码也公开在了[https://github.com/LiPtP0000/POC\\_Design](https://github.com/LiPtP0000/POC_Design), 可能相比报告中的代码有微小的改动。

### A.1 top.v

```
module TOP (
    i_clk,
    i_rst_n,
    i_data,
    i_mode,
    o_tr,
    o_pd,
    o_rdy,
    o_data,
    o_rw,
    o_addr,
    o_irq,
    o_data_poc_to_processor,
    o_data_processor_to_poc
);
// I/O

input wire i_clk;
input wire i_rst_n;
input wire i_mode;
input wire [7:0] i_data;

output wire [7:0] o_data;
output wire o_irq;
output wire o_addr;
output wire o_rw;
output wire o_tr;
output wire [7:0] o_pd;
output wire o_rdy;
output wire [7:0] o_data_poc_to_processor;
```

```

output wire [7:0] o_data_processor_to_poc;
// CPU/POC connections

wire irq;
wire addr;
wire [7:0] data_processor_to_POC;
wire [7:0] data_POC_to_processor;
wire rw;

// POC/Printer connections

wire tr;
wire [7:0] pd;
wire rdy;

// Instantiations

PROCESSOR u_processor (
    .i_clk(i_clk),           // 时钟输入
    .i_rst_n(i_rst_n),       // 复位信号，低有效
    .i_irq(irq),              // 中断
    .i_data(i_data),          // Directly from TB
    .i_dout(data_POC_to_processor), // 从 POC 读取的数据
    .o_din(data_processor_to_POC), // 发送到 POC 的数据
    .o_addr(addr),            // 地址信号
    .o_rw(rw)                 // 读/写信号
);

POC u_poc (
    .i_addr(addr),
    .o_dout(data_POC_to_processor),
    .i_din(data_processor_to_POC),
    .i_rw(rw),
    .i_clk(i_clk),
    .i_rst_n(i_rst_n),
    .i_mode(i_mode),
    .o_irq(irq),
    .i_rdy(rdy),
    .o_tr(tr),
    .o_pd(pd)
);

PRINTER u_printer (
    .i_tr(tr),
    .i_pd(pd),
    .o_rdy(rdy),
    .i_clk(i_clk),
    .i_rst_n(i_rst_n),
    .o_data(o_data)           // directly output to tb
);

// assignments

// CPU/POC

```

```

assign o_irq = irq;
assign o_addr = addr;
assign o_rw = rw;
assign o_data_processor_to_poc = data_processor_to_POC;
assign o_data_poc_to_processor = data_POC_to_processor;

// POC/Printer
assign o_tr = tr;
assign o_pd = pd;
assign o_rdy = rdy;

endmodule

```

## A.2 poc.v

```

module POC (
    i_addr,
    o_dout,
    i_din,
    i_rw,
    i_clk,
    i_rst_n,
    i_mode,
    o_irq,
    i_rdy,
    o_tr,
    o_pd
);

// From Top module

input wire i_mode; // 0 = query, 1 = interrupt

// From/to Processor

input wire i_addr; // 0: status, 1: buffer
input wire i_clk;
input wire i_rst_n;
input wire i_rw; // 0: read, 1: write
input wire [7:0] i_din; // status/data from Processor
output wire [7:0] o_dout; // status to CPU
output wire o_irq; // 0: interrupt

// From/to Printer
input wire i_rdy;
output wire o_tr;
output [7:0] o_pd;

// Inside POC
reg mode;
reg [7:0] status;
reg [7:0] buffer;

```

```

reg [7:0] printer_data;
reg enable_printer;
wire interrupt;
reg ready;

// State Params

parameter IDLE = 3'b0;
// Wait for CPU response
parameter POLLING_CPU_WRITE = 3'b001;
// POC will receive data from processor using polling method
parameter POLLING_TO_PRINTER = 3'b010;
// POC will transmit data to printer
parameter INTERRUPT_CPU_WRITE = 3'b011;
// POC will receive data from processor using interrupt method
parameter INTERRUPT_TO_PRINTER = 3'b100;
// POC will transmit data to printer

reg [2:0] state, next_state;

// initial
always @(posedge i_clk or negedge i_rst_n) begin
    if (!i_rst_n) begin
        state <= IDLE;
        ready <= 'b0; // maybe there is a more beautiful solution
        mode <= 'b0;
    end else begin
        state <= next_state;
        ready <= i_rdy;
        mode <= i_mode;
    end
end

// state transition
always @(*) begin
    case (state)
        IDLE: begin
            if (i_rw == 1'b1) begin
                if (status[0] == 0) begin // query
                    next_state = POLLING_CPU_WRITE;
                end else begin
                    if (interrupt == 1'b1) begin
                        next_state = INTERRUPT_CPU_WRITE;
                    end
                end
            end else begin
                next_state = IDLE;
            end
        end
        POLLING_CPU_WRITE: begin

```

```

        if (status[7] == 0) begin
            next_state = POLLING_TO_PRINTER;
        end else begin
            next_state = POLLING_CPU_WRITE;
        end
    end
end
POLLING_TO_PRINTER: begin
    if (i_rdy == 'b1 && ready == 'b0) begin
        next_state = IDLE;
    end else begin
        next_state = POLLING_TO_PRINTER;
    end
end
INTERRUPT_CPU_WRITE: begin
    if (status[7] == 0) begin
        next_state = INTERRUPT_TO_PRINTER;
    end else begin
        next_state = INTERRUPT_CPU_WRITE;
    end
end
INTERRUPT_TO_PRINTER: begin
    if (i_rdy == 'b1 && ready == 'b0) begin
        next_state = IDLE;
    end else begin
        next_state = INTERRUPT_TO_PRINTER;
    end
end
default: begin
    next_state = IDLE;
end
endcase
end

// status and buffer
always @(*) begin
    case (state)
        IDLE: begin
            status      = {7'b1000000, mode}; // reset to POC ready
            printer_data = 8'b0; // every cycle reset the printer data
            enable_printer = 1'b0; // every cycle reset the printer status
        end
        POLLING_CPU_WRITE: begin
            // CPU needs to write both buffer and status in this state
            if (i_rw == 1'b1 && i_addr == 1'b1) begin
                buffer = i_din;
            end
            if (i_rw == 1'b1 && i_addr == 1'b0) begin
                status = i_din;
            end
        end
        INTERRUPT_CPU_WRITE: begin
            if (i_rw == 1'b1 && i_addr == 1'b1) begin
                buffer = i_din;
            end
        end
    end
end

```

```

        end
        if (i_rw == 1'b1 && i_addr == 1'b0) begin
            status = i_din;
        end
    end
endcase
end

always @(posedge i_clk or negedge i_rst_n) begin
    if (!i_rst_n) enable_printer <= 1'b0;
    else begin
        if (state == POLLING_TO_PRINTER || state == INTERRUPT_TO_PRINTER) begin

            if (ready == 1'b1 && enable_printer == 1'b0) begin
                printer_data <= buffer;
                enable_printer <= 1'b1;
            end else if (enable_printer == 1'b1) begin
                enable_printer <= 1'b0;
            end
        end
    end
end

// Assignments
assign o_irq = ~interrupt;
assign o_tr = enable_printer;
assign o_pd = printer_data;
assign o_dout = status;

assign interrupt = status[7] & status[0];

endmodule

```

### A.3 processor.v

```

module PROCESSOR (
    i_clk,
    i_rst_n,
    i_irq,
    i_dout,
    i_data,
    o_din,
    o_addr,
    o_rw
);

input wire i_clk;
input wire i_rst_n;
input wire i_irq;
input wire [7:0] i_dout; // Data from POC (specifically status info)
input wire [7:0] i_data; // Data from top module

```

```

output reg [7:0] o_din; // Data to POC
output wire o_addr;
output wire o_rw;

// Internal registers
reg [7:0] poc_status;
reg address;
reg rw;

// State registers
reg [2:0] state, next_state;

// Status tracking signals
reg set_data_done;
reg read_status_done;

// Mode signal from poc_status[0]
wire mode = poc_status[0];
wire interrupt = i_irq;

// State encoding
parameter STATUS = 1'b0;
parameter BUFFER = 1'b1;

parameter IDLE = 3'b000;
parameter READ_FROM_POC = 3'b001;
parameter SET_DATA = 3'b010;
parameter WRITE_DATA = 3'b011;
parameter DELAY = 3'b100;
parameter WRITE_STATUS = 3'b101;

// State transition
always @(posedge i_clk or negedge i_rst_n) begin
    if (!i_rst_n) state <= IDLE;
    else state <= next_state;
end

// Next state logic
always @(*) begin
    case (state)
        IDLE: begin
            if (mode == 1'b0) next_state = READ_FROM_POC;
            else if (interrupt == 1'b0) next_state = SET_DATA;
            else next_state = IDLE;
        end
        READ_FROM_POC: begin
            if (read_status_done && poc_status[7] == 1'b1) next_state = SET_DATA;
            else next_state = READ_FROM_POC;
        end
        SET_DATA: begin
            if (set_data_done) next_state = WRITE_DATA;
            else next_state = SET_DATA;
        end
        WRITE_DATA: begin

```



```

        next_state = DELAY; // wait one clock cycle for poc read delay
    end
    DELAY: begin
        next_state = WRITE_STATUS;
    end
    WRITE_STATUS: begin
        next_state = IDLE;
    end
    default: next_state = IDLE;
endcase
end

// Control logic for address and rw
always @(*) begin
    case (state)
        IDLE: begin
            address = STATUS;
            rw = 1'b0;
        end
        READ_FROM_POC: begin
            rw = 1'b0;
            address = STATUS;
        end
        SET_DATA: begin
            rw = 1'b0;
            address = BUFFER;
        end
        WRITE_DATA: begin
            rw = 1'b1;
            address = BUFFER;
        end
        WRITE_STATUS: begin
            rw = 1'b1;
            address = STATUS;
        end
    endcase
end

// Output data control
always @(*) begin
    set_data_done = 1'b0;
    if (state == WRITE_DATA || state == IDLE) begin
        set_data_done = 1'b0;
    end else begin
        if (address == STATUS) o_din = poc_status;
        else begin
            o_din = i_data;
            set_data_done = 1'b1;
        end
    end
end

// poc_status and read_status_done update
always @(posedge i_clk or negedge i_rst_n) begin

```

```

    if (!i_rst_n) begin
        read_status_done <= 1'b0;
        poc_status <= 8'b0;
    end else begin
        case (state)
            IDLE: begin
                read_status_done <= 1'b0;
            end
            READ_FROM_POC: begin
                poc_status <= i_dout;
                read_status_done <= 1'b1;
            end
            SET_DATA: begin
                poc_status[7] <= 1'b0;
            end
        endcase
    end
end

// Assign output signals
assign o_rw    = rw;
assign o_addr = address;

endmodule

```

## A.4 printer.v

```

module PRINTER (
    i_tr,
    i_pd,
    o_rdy,
    i_clk,
    i_rst_n,
    o_data
);
    // interfaces
    input wire i_clk;
    input wire i_rst_n;
    input wire i_tr;
    input wire [7:0] i_pd;
    output wire o_rdy;
    output wire [7:0] o_data;

    // inside printer
    reg [7:0] delay_buffer[0:3]; // for delaying 4 cycles
    reg [2:0] count;
    reg state, next_state;

    parameter IDLE = 1'b0;
    parameter BUSY = 1'b1;

    always @(posedge i_clk or negedge i_rst_n) begin

```

```

    if (!i_rst_n) begin
        state <= IDLE;
    end else begin
        state <= next_state;
    end
end

// state transition
always @(*) begin
    case (state)
        IDLE: begin
            if (i_tr) begin
                next_state <= BUSY;
            end else begin
                next_state <= IDLE;
            end
        end
        BUSY: begin
            // we will wait 8 clock cycles for printer to print, even though the printing process
            // only needs 4.
            if (count == 3'b111) begin
                next_state <= IDLE;
            end else begin
                next_state <= BUSY;
            end
        end
        default: begin
            next_state <= IDLE;
        end
    endcase
end

// counter
always @(posedge i_clk or negedge i_rst_n) begin
    if (!i_rst_n) begin
        count <= 3'b0;
    end else begin
        case (state)
            IDLE: begin
                count <= 3'b0;
            end
            BUSY: begin
                count <= count + 1;
            end
            default: begin
                count <= 3'b0;
            end
        endcase
    end
end

// delay four cycles to simulate printing process
always @(posedge i_clk) begin

```

```

    if (state == BUSY) begin
        delay_buffer[0] <= i_pd;
    end
end

always @(posedge i_clk) begin
    if (state == BUSY) begin
        delay_buffer[1] <= delay_buffer[0];
    end
end

always @(posedge i_clk) begin
    if (state == BUSY) begin
        delay_buffer[2] <= delay_buffer[1];
    end
end

always @(posedge i_clk) begin
    if (state == BUSY) begin
        delay_buffer[3] <= delay_buffer[2];
    end
end

assign o_data = delay_buffer[3];
assign o_rdy  = (state == IDLE) ? 1'b1 : 1'b0;

endmodule

```

## A.5 tb.v

```

// Date: 2025.3.10
// Author: LiPtP
// Description: Testbench for TOP module
`timescale 1ns / 1ps
module tb_POC;

    // Clock and reset
    reg clk;
    reg reset;

    // Input to modules
    reg [7:0] data_in;
    reg mode;

    // Output from modules
    wire [7:0] printer_data;
    wire printer_tr;
    wire [7:0] poc_pd;
    wire poc_ready;

    wire rw;
    wire addr;
    wire [7:0] data_POC_to_processor;

```

```

wire [7:0] data_processor_to_POC;
wire irq_n;

// Clock generation (50MHz, 20ns period)
always #10 clk = ~clk;

// Reset sequence
initial begin
    clk = 0;
    reset = 0;
    mode = 0;
    data_in = 8'b0;

    #50 reset = 1; // 50ns delay to allow reset propagation
end

// Mode switching after 100,000 ns
initial begin
    #100000 mode = 1;
end

// Periodic Data Input
initial begin
    #100;
    while (1) begin
        if (mode == 0) begin
            data_in = 8'b00000000;
            #340;
            data_in = 8'b00000001;
            #340;
            data_in = 8'b00000010;
            #340;
            data_in = 8'b00000011;
            #340;
            data_in = 8'b00000100;
            #340;
            data_in = 8'b00000101;
            #340;
            data_in = 8'b00000110;
            #340;
            data_in = 8'b00000111;
            #340;
            data_in = 8'b00001000;
            #340;
            data_in = 8'b00001001;
            #340;
            data_in = 8'b00001010;
            #340;
            data_in = 8'b00001011;
            #340;
            data_in = 8'b00001100;
            #340;
            data_in = 8'b00001101;
            #340;
        end
    end
end

```

```

data_in = 8'b00001110;
#340;
data_in = 8'b00001111;
#340;
data_in = 8'b00010000;
#340;
data_in = 8'b00010001;
#340;
data_in = 8'b00010010;
#340;
data_in = 8'b00010011;
#340;
data_in = 8'b00010100;
#340;
end else begin
data_in = 8'b00000000;
#320;
data_in = 8'b00000001;
#320;
data_in = 8'b00000010;
#320;
data_in = 8'b00000011;
#320;
data_in = 8'b00000100;
#320;
data_in = 8'b00000101;
#320;
data_in = 8'b00000110;
#320;
data_in = 8'b00000111;
#320;
data_in = 8'b00001000;
#320;
data_in = 8'b00001001;
#320;
data_in = 8'b00001010;
#320;
data_in = 8'b00001011;
#320;
data_in = 8'b00001100;
#320;
data_in = 8'b00001101;
#320;
data_in = 8'b00001110;
#320;
data_in = 8'b00001111;
#320;
data_in = 8'b00010000;
#320;
data_in = 8'b00010001;
#320;
data_in = 8'b00010010;
#320;
data_in = 8'b00010011;

```

```

        #320;
        data_in = 8'b00010100;
        #320;

    end
end
end

// Dump waveforms
initial begin
    $dumpfile("poc.vcd");
    $dumpvars(0, tb_POC);
    #200000 $finish;
end

// Instantiate DUT
TOP u_dut (
    .i_clk(clk),
    .i_rst_n(reset),
    .i_data(data_in),
    .i_mode(mode),
    .o_tr(printer_tr),
    .o_pd(poc_pd),
    .o_rdy(poc_ready),
    .o_data(printer_data),
    .o_rw(rw),
    .o_addr(addr),
    .o_irq(irq_n),
    .o_data_poc_to_processor(data_POC_to_processor),
    .o_data_processor_to_poc(data_processor_to_POC)
);

endmodule

```